
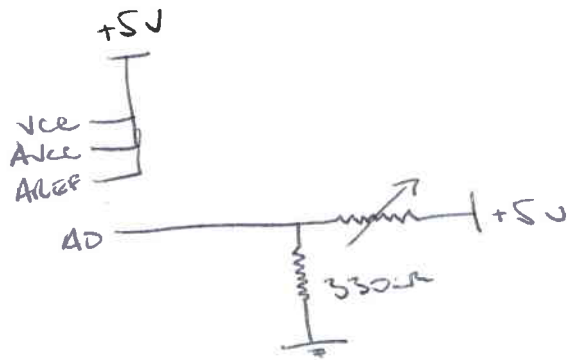



HLT

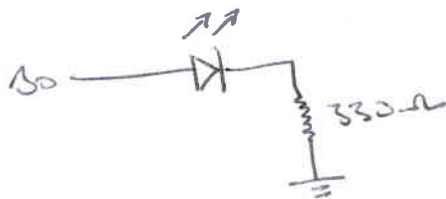

Simulated TEMPERATURE
sensor using POTENTIOMETER
AND RESISTOR.



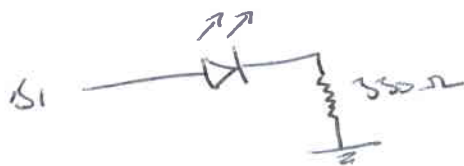Simulated ELECTRIC HEATER
ELEMENT using AN LED
AND A RESISTOR





Simulated VALVE using
AN LED AND A RESISTOR




Flow sensor is correctly
simulated with a TIMER.



MASH TON

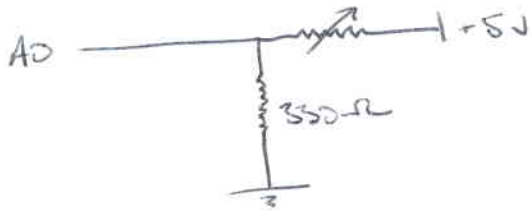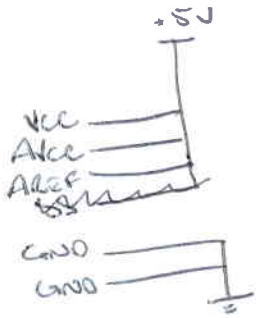

~~On~~ \rightarrow to STEPPER

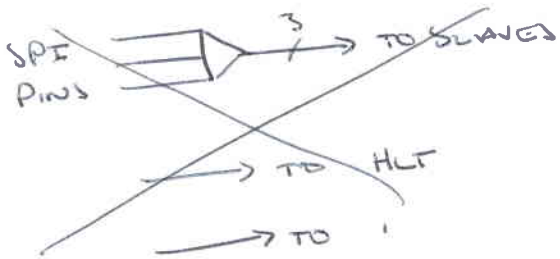

Current-1 Setup

Port A : ADC (A0), NOT EMPTY SWITCH (A1)

FULL BUTTON (A2)

PORT B: HEAT LED (130)

NOT EMPTY LED (B1)

Full LED (B2)

PORT C : STEPPER MOTOR (C[3:0])

Simulated Temperature
Sensor using Potentiometer
And Resistor.

SIMULATED FLOAT SWITCH
USING A NORMAL SWITCH.





DRIPPER MOTOR DRIVES THE MIXING ARM, WHICH IS CONSTANTLY SPINNING WHILE THE WASH TUB IS FULL, OR IN USE.

Boil Kettle

SETUP

PORT A: ADC, POT (A1)

PORT B: HEAT LED (B0)

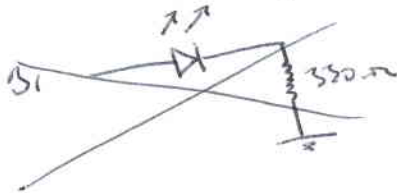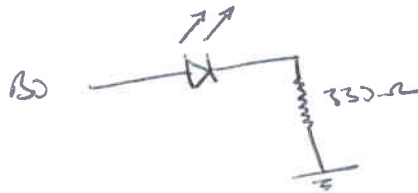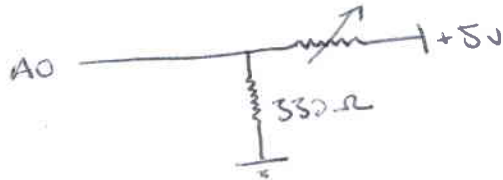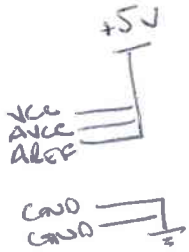


Simulated Temperature sensor using Potentiometer and Resistor.

Simulated Electric Heating Element using an LED and a Resistor.

Flow sensor is completely simulated with a timer.

TEST MASTER

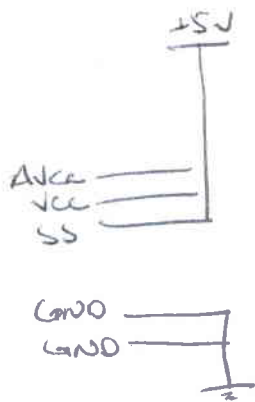

B0 → TO HLT

B1 → TO MT

B2 → TO DIL



A0 ~~AK~~ — \perp — \vdash

A1 — \perp — \vdash

A2 — \perp — \vdash

A3 — \perp — \vdash

HLT

HEAT WATER

PERSISTENT HEAT WATER

MT

~~WASH~~ ^{START} ~~WASH~~ WASH

DIL

START DIL